

Embedded Systems

Prof. Dr. Volker Strumpen

Rhine-Waal University of Applied Sciences

Winter Semester 2019

Syllabus

No	Date	Topic
1	10/2	Introduction
2	10/9	Facing the World
3	10/16	Sensors
4	10/23	Actuators
5	10/30	AVR Architecture
6	11/6	MCU System Architecture
7	11/13	C Programming
8	11/20	Assembly Programming
9	11/27	Timers and Interrupts
10	12/4	Communication
11	12/11	Real-Time Systems
12	12/18	Scheduling
13	1/8	Modeling
14	1/15	Model Checking

Outline


- Models of Actuators
- LED
- Piezoceramic Element
- DC Motor
- Servo Motor

Models of Actuators

We use actuators to alter a physical quantity. As for sensors, proper use of an actuator relies on practical experience and a model that is good enough for the intended application.

LED diode: Recall the digital model of an LED as a switch
 
$$\text{diode switch} = \begin{cases} \text{closed (LED on)}, & V_{LED} \geq V_B, \\ \text{open (LED off)}, & V_{LED} < V_B \end{cases}$$




Models of Actuators

Q: Do LEDs with different colors behave like red LEDs?

A: No. Different colors originate from different materials that emit photons at different wavelengths, and affect the forward-bias voltage of the diode.

Typical LED characteristics:

Color	$\lambda[nm]$	V_{20mA}	Material
red	630–660	2.1V	GaAsP
yellow	580–590	2.3V	AlGaInP
green	550–570	2.5V	AlGaP
blue	450–500	3.2V	SiC

 


Note: Analog diode models have exponential IV-characteristics.

Models of Actuators

A **DC motor** is an actuator that converts electrical into mechanical energy and vice versa:

 - Spin the shaft and you can measure a voltage at the terminals.
- Apply a voltage and the shaft spins.
- Apply the opposite voltage and the shaft spins in the opposite direction.




Models of Actuators

A piezoceramic element, **piezo** for short, functions as a loudspeaker or buzzer that generates air pressure.

We can model a piezo as a resonant RLC circuit. However, the resonant peak is not as distinguished in the measured frequency response as in an ideal RLC circuit:

no model is perfect

 

Practice: The resonant frequency of a buzzer is where it is loudest.

Models of Actuators

A DC motor can be modeled with the fundamental laws of physics:


- The torque (rotational force) that acts on the shaft of a motor at rest is proportional to the current through the coils:

$$T(t) = k_T i(t)$$

- If the motor spins with angular velocity ω , the magnetic field induces a back electromotive force, **back EMF** for short, that opposes the rotation:

$$E_b(t) = k_e \omega(t)$$

 - The maximum torque T_0 acts on the stalled shaft when $\omega = 0$.
- When the motor rotates at maximum velocity ω_0 then torque $T = 0$.



Models of Actuators

Assume the coil has resistance R and inductance L .

- The voltage at the coil terminals of a DC motor is:

$$v(t) = Ri(t) + L \frac{di(t)}{dt} + E_b$$

- For constant current $i(t) = T/k_t$ and $v(t) = V$, the motor spins at constant speed

$$\omega_m = \frac{V}{k_e} - \frac{RT}{k_e k_t}$$

- Let J be the moment of inertia of the shaft including load, then Newton's law ($F = ma$) for rotations is:


$$T(t) = J \frac{d\omega(t)}{dt}$$

- Applying a voltage V_0 to the motor at rest creates torque T_0 , and the motor speed increases asymptotically

$$\omega(t) = \frac{k_T T_0}{k_e R} \left(1 - e^{-\frac{k_e R}{J k_T} t}\right)$$

Models of Actuators

 Motor response to input voltage step $v(t) = V_0 u(t)$:



Models of Actuators

Q: How can we adjust the speed (RPM) of the motor?

A1: Relation $\omega_m(V)$: increase voltage V to increase ω_m .

Problem: Our model does not capture a second-order effect, friction.


When the motor is at rest, friction prevents the motor from starting if the voltage is too low.

A2: Pulse width modulation (PWM) with nominal voltage.

The inertia of the motor and mechanical load suffices to smooth out abrupt changes of the voltage, e.g. when applying a square wave.


Models of Actuators

 PWM enables us to control the motor speed. The larger the duty cycle, the faster the motor spins:




Models of Actuators

 PWM enables us to control the motor speed. The larger the duty cycle, the faster the motor spins:



Models of Actuators

 PWM enables us to control the motor speed. The larger the duty cycle, the faster the motor spins:



DC Motor Control


An MCU like an Arduino cannot drive a DC motor directly, because

- the DC motor requires a voltage of 9 V, whereas the maximum voltage on the Arduino Uno board is 5 V,
- the DC motor draws more current than an Arduino pin can supply.

We use a power MOSFET NPN transistor (IRF520) that can tolerate voltages up to $V_{DS} = 100$ V and currents up to $I_D = 9.7$ A.

An Arduino pin can drive the gate of the transistor, i.e. a capacitor.

 Operation: The Arduino PWM pin outputs a square wave that operates the transistor as a digital switch. The transistor isolates the Arduino from the high-voltage/high-current motor circuit.




DC Motor Control

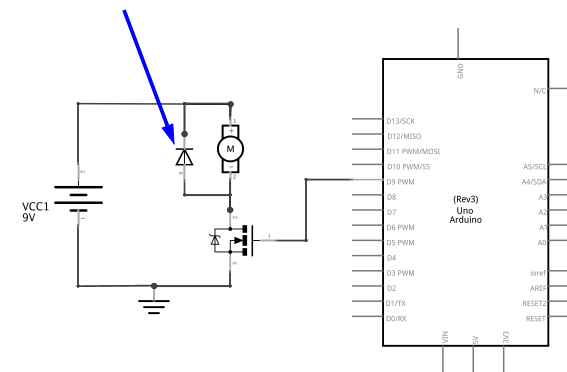Problem: When a DC motor is switched off, the inductance continues to drive a current, that can build up a damaging voltage.




We add a **flyback diode**, aka **snubber diode**, in parallel to the motor to provide a path for dissipating the induced current.



DC Motor Control

 Arduino circuit uses pin 9 for PWM output:




Careful: The power MOSFET can get very hot!

Arduino Sketch: DC Motor Speed Control


```
int pwmctrl = 128; // must be in [0, 255] for analogWrite
void setup() { Serial.begin(9600); }
void loop() {
    int newpwm = pwmctrl;
    while (Serial.available() > 0) {
        int c = Serial.read();
        if (c == '+' && newpwm < 255)
            newpwm++;
        if (c == '-' && newpwm > 0)
            newpwm--;
    }
    if (newpwm != pwmctrl) {
        pwmctrl = newpwm;
        Serial.print("pwmctrl = ");
        Serial.println(pwmctrl);
        analogWrite(9, pwmctrl); // adjust motor speed
    }
    delay(10);
}
```

DC Motor Control

 To control both speed and direction of a motor without modifying the circuit, we need four switches:



Forward rotation

 


Backward rotation

This circuit is an **H-Bridge**. It is available as an IC with support for PWM speed control, and includes snubber diodes.

DC Motor Control

Pin assignment of H-bridge part L293D:

 

L293D features and connections:

- Two H-bridges for two motors. Apply a PWM signal to pin *en1* and/or *en2* for speed control of each motor.
- Pins *out1* and *out2* drive one DC motor directly. Pins *out3* and *out4* can drive a second motor.
- Supply 5 V to pin 16 to power the H-bridge, and 9 V to pin 8 which serves as power supply for the DC motors.

DC Motor Control

Motor control with L293D:


- The motor driven by pins *out1* and *out2* is speed controlled by PWM pin *en1*.
- The motor direction is selected via digital pins *in1* and *in2* according to the truth table:

<i>in1</i>	<i>in2</i>	Motor action
LOW	LOW	stop
HIGH	LOW	forward
LOW	HIGH	backward
HIGH	HIGH	stop

- A second motor can be speed controlled by PWM pin *en2*, and the direction is selected via digital pins *in3* and *in4*.

DC Motor Control

 DC motor control with Arduino and H-bridge:



Arduino Sketch: DC Motor Control with H-Bridge

```
#define STOP 0 // motor directions
#define FWD 1
#define BWD 2

int dir = STOP; // stop initially
int pwmctrl = 128; // must be in range [0, 255] for analogWrite

void setup() {
  Serial.begin(9600);
  analogWrite(10, pwmctrl);
}

void loop() {
  int newpwm = pwmctrl;
  int newdir = dir;
  while (Serial.available() > 0) { // receive cmd from host
    int c = Serial.read();
    switch (c) {
      case 's':
        newdir = STOP;
        break;
    }
  }
}
```

Arduino Sketch: DC Motor Control with H-Bridge

```
case 'f':
  newdir = FWD;
  break;
case 'b':
  newdir = BWD;
  break;
case '+':
  if (newpwm < 255)
    newpwm++;
  break;
case '-':
  if (newpwm > 0)
    newpwm--;
  break;
}
/* end while*/
if (newdir != dir) { // set new direction
  switch (newdir) {
```

Arduino Sketch: DC Motor Control with H-Bridge

```
case STOP:
  Serial.println("stop motor");
  digitalWrite(7, LOW);
  digitalWrite(8, LOW);
  break;
case FWD:
  Serial.println("spin forward");
  digitalWrite(7, LOW);
  digitalWrite(8, HIGH);
  break;
case BWD:
  Serial.println("spin backward");
  digitalWrite(7, HIGH);
  digitalWrite(8, LOW);
  break;
}
dir = newdir;
} /* endif set new direction */
```


Arduino Sketch: DC Motor Control with H-Bridge

```
if (newpwm != pwmctrl) {           // set new speed
  pwmctrl = newpwm;
  Serial.print("pwmctrl = ");
  Serial.println(pwmctrl);
  analogWrite(10, pwmctrl);        // adjust motor speed
}
delay(10);
}
```

Careful: Stop the motor before reversing direction at high speed.

Servo Motor

 
A **servo motor** is a DC motor with an electrical feedback loop to control the position of the shaft with a PWM signal:



- Servo motors do not spin, but can lock the shaft into position.
- The gear box includes a mechanical position sensor, a cogwheel that turns a potentiometer.
- **Affine model:** The shaft position, i.e. the angle of the shaft, is proportional to the duty cycle of the PWM input, and the angle is limited to interval $[0^\circ, 180^\circ]$.

Servo Motor Control

Servo motor control with Arduino:

 

Decoupling capacitor (decap): The $100\mu\text{F}$ electrolytic capacitor buffers current spikes when the servo turns on. Capacitive decoupling prevents voltage dips on the Arduino board that could otherwise result in malfunctioning of the MCU.

Arduino Sketch: Servo Motor Control

```
#include <Servo.h> // use Arduino Servo library
Servo servomotor; // instantiate Servo object
int angle = 90;    // must be in range [0, 179] for Servo.write

void setup() {
  servomotor.attach(3); // attach pwm pin 3
  Serial.begin(9600);
}

void loop() {
  int newangle = angle;
  while (Serial.available() > 0) { // receive cmd from host
    int c = Serial.read();
    if (c == '+' && newangle < 179)
      newangle++;
    if (c == '-' && newangle > 0)
      newangle--;
  }
}
```

Arduino Sketch: Servo Motor Control

```
if (newangle != angle) {
  angle = newangle;
  Serial.print("angle = ");
  Serial.println(angle);

  servomotor.write(angle); // adjust angle
}

delay(10);
}
```